
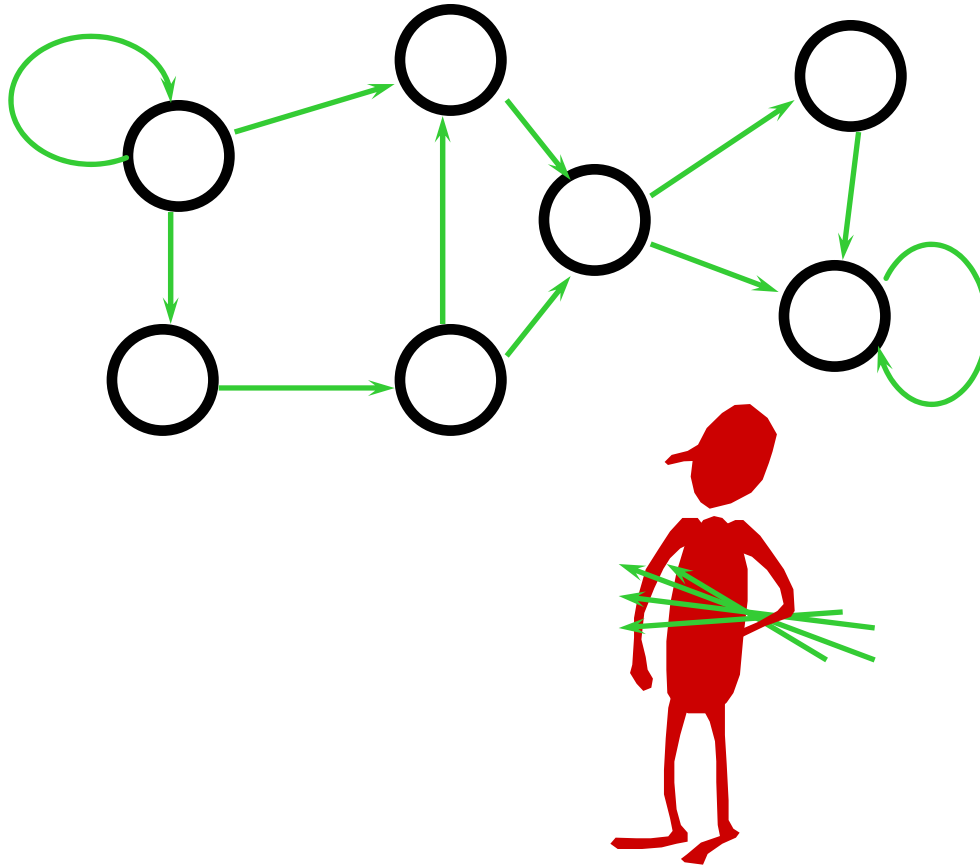


Sequential Logic

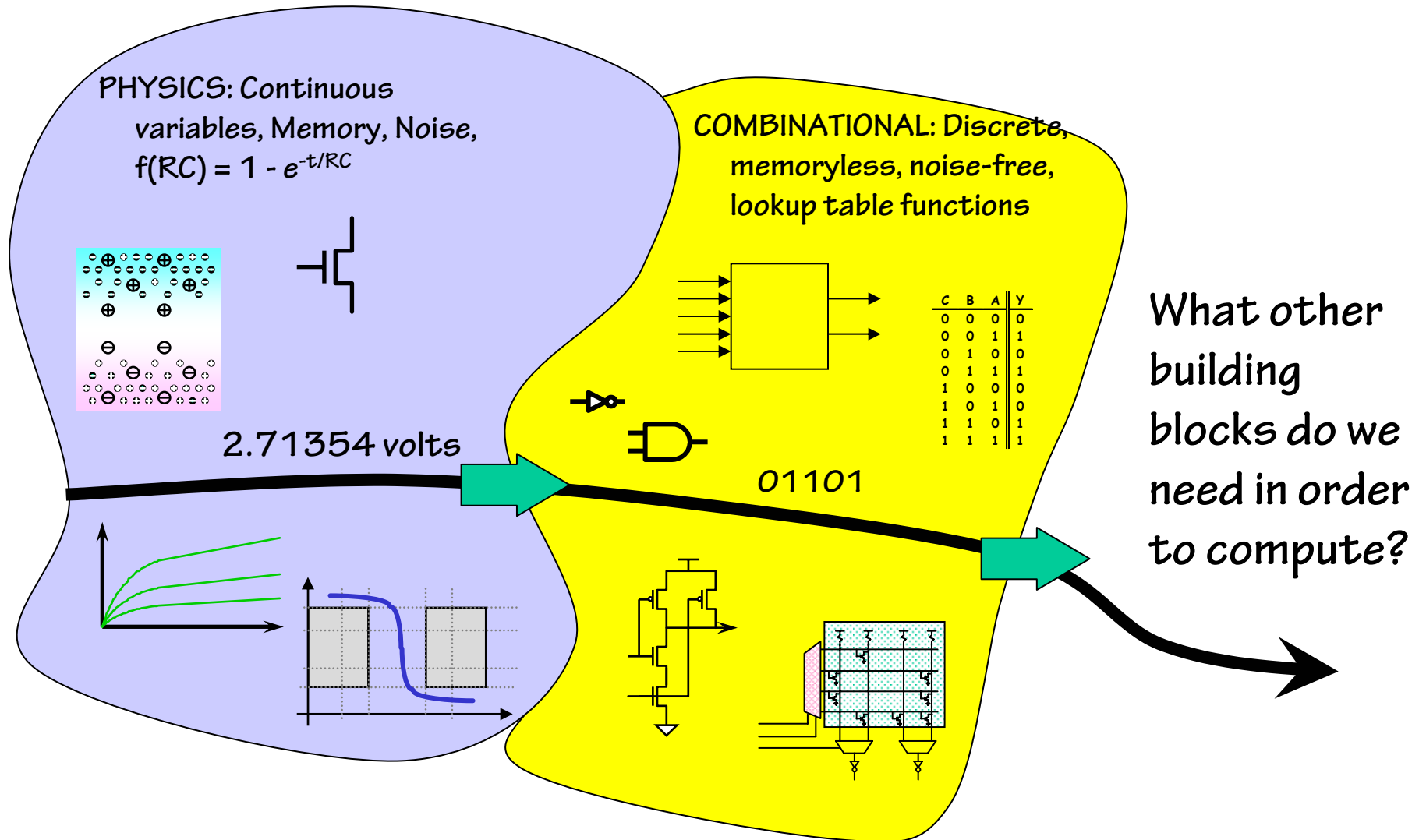


Handouts: Lecture Slides

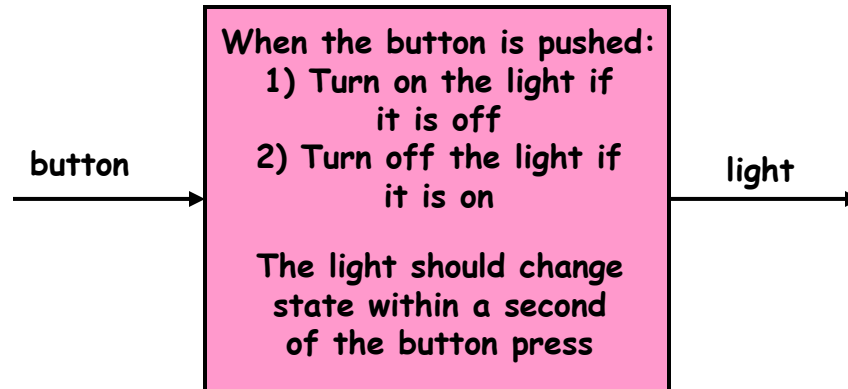6.004: Progress so far...



Something We Can't Build (Yet)

What if you were given the following design specification:




What makes this circuit so different from those we've discussed before?

1. "State" – i.e. the circuit has memory
2. The output was changed by a input "event" (pushing a button) rather than an input "value"

Digital State

One model of what we'd like to build

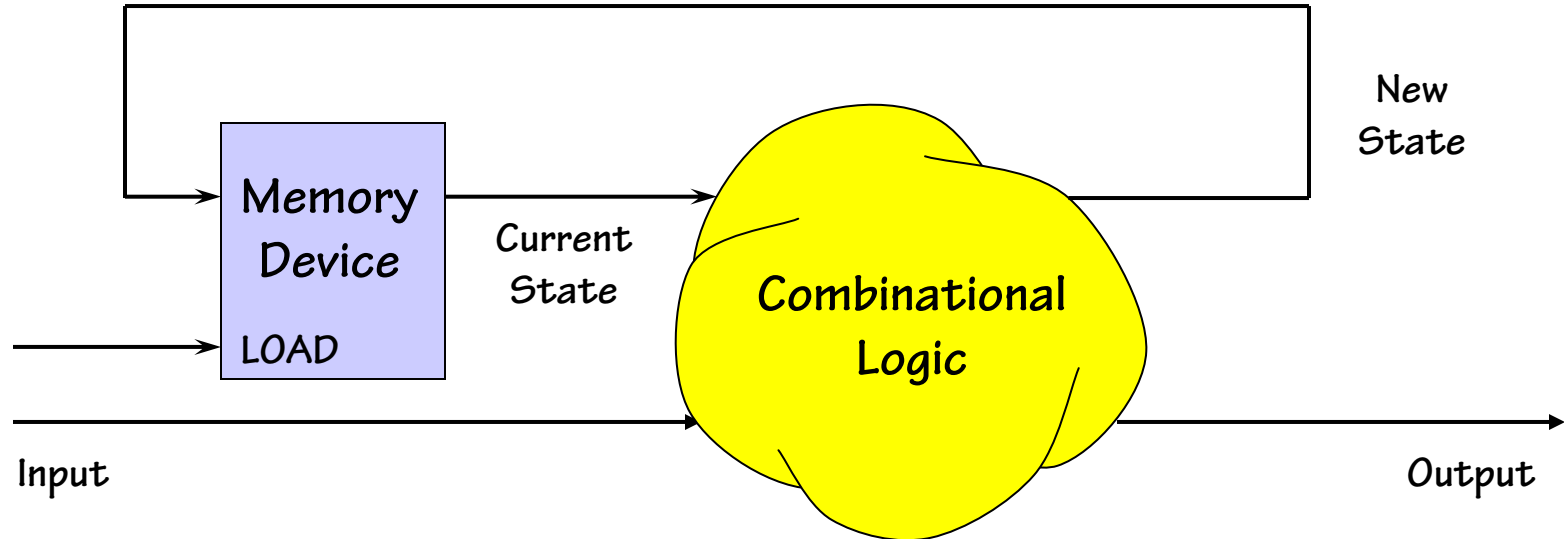

Plan: Build a Sequential Circuit with stored digital STATE -

- Memory stores CURRENT state, produced at output
- Combinational Logic computes
 - NEXT state (from input, current state)
 - OUTPUT bit (from input, current state)
- State changes on LOAD control input

Needed: *Storage*

Combinational logic is *stateless*:

valid outputs always reflect current inputs.

To build devices with state, we need components which *store* information (e.g., state) for subsequent access.

ROMs (and other combinational logic) store information “wired in” to their truth table


Read/Write memory elements are required to build devices capable of changing their contents.

How can we store – and subsequently access -- a bit?

- Mechanics: holes in cards/tapes
- Optics: Film, CDs, DVDs, ...
- Magnetic materials
- Delay lines; moonbounce
- Stored charge

Storage: Using Capacitors

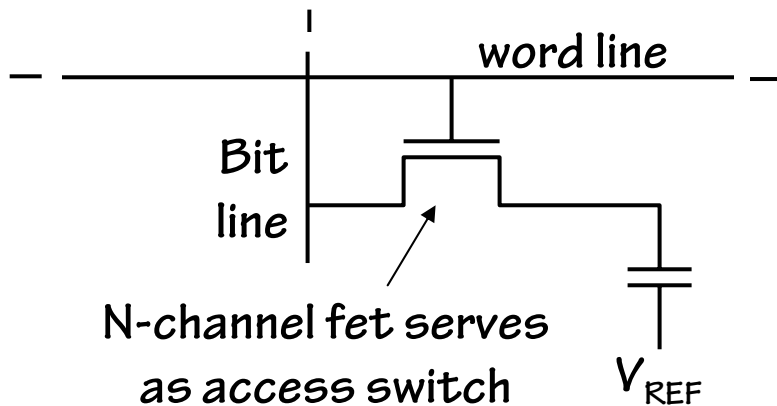We've chosen to encode information using voltages and we know from 6.002 that we can "store" a voltage as charge on a capacitor:



To write:

Drive bit line, turn on access fet,
force storage cap to new voltage

To read:

precharge bit line, turn on access fet,
detect (small) change in bit line voltage

Pros:

- ◆ compact – low cost/bit (on BIG memories)


Cons:

- ◆ complex interface
- ◆ stable? (noise, ...)
- ◆ it leaks! \Rightarrow refresh


Suppose we refresh
CONTINUOUSLY?

Storage: Using Feedback

 IDEA: use **positive feedback** to maintain storage indefinitely.
Our logic gates are built to restore marginal signal levels, so noise shouldn't be a problem!



Result: a **bistable storage element**

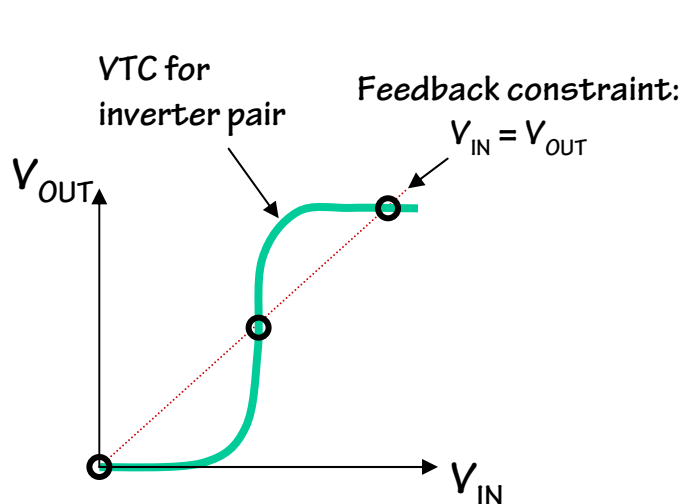

Not affected
by noise


Three solutions:

- ◆ two end-points are **stable**
- ◆ middle point is unstable

We'll get back to this!

Settable Storage Element


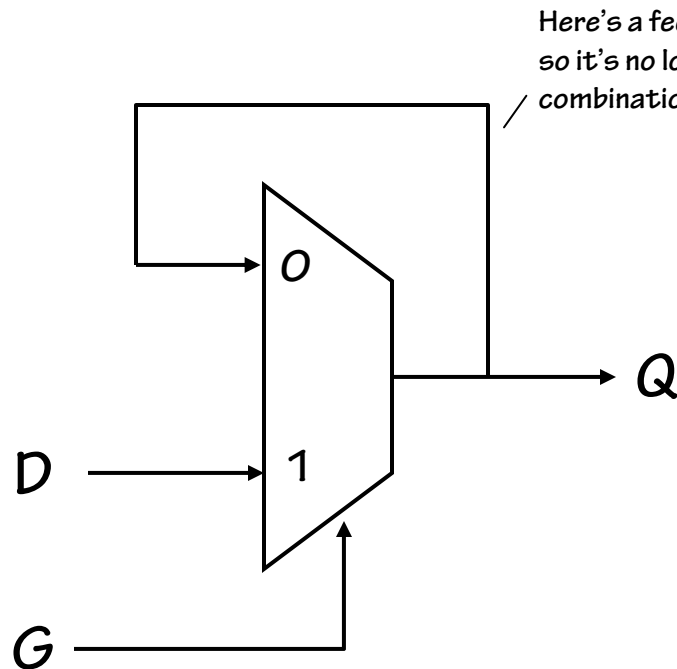
It's easy to build a settable storage element (called a **latch**) using a *lenient* MUX:



"state" signal appears as both input and output

G	D	Q_{IN}	Q_{OUT}	
0	--	0	0	} Q stable
0	--	1	1	
1	0	--	0	} Q follows D
1	1	--	1	

New Device: D Latch

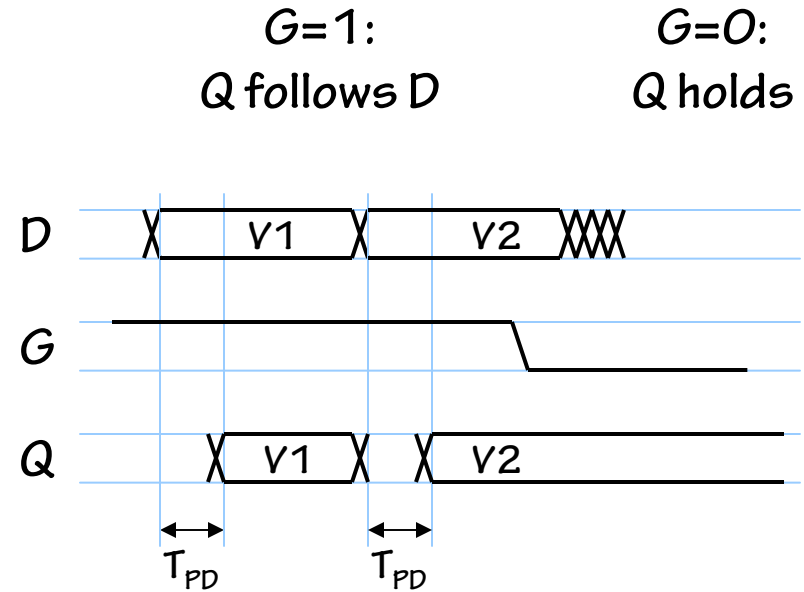
 


BUT... A change in D or G contaminates Q , hence Q' ... how can this possibly work?

$G=1$: Q Follows D , independently of Q'

$G=0$: Q Holds stable Q' , independently of D


A Plea for Lenience...

  

Assume LENIENT Mux, propagation delay of T_{PD}

Then output valid when


 
- $G=1$, D stable for T_{PD} , independently of Q' ;
or
- $Q'=D$ stable for T_{PD} , independently of G ; or
- $G=0$, Q' stable for T_{PD} , independently of D



Does lenience *guarantee* a working latch?

What if D and G change at about the same time...

... with a little discipline

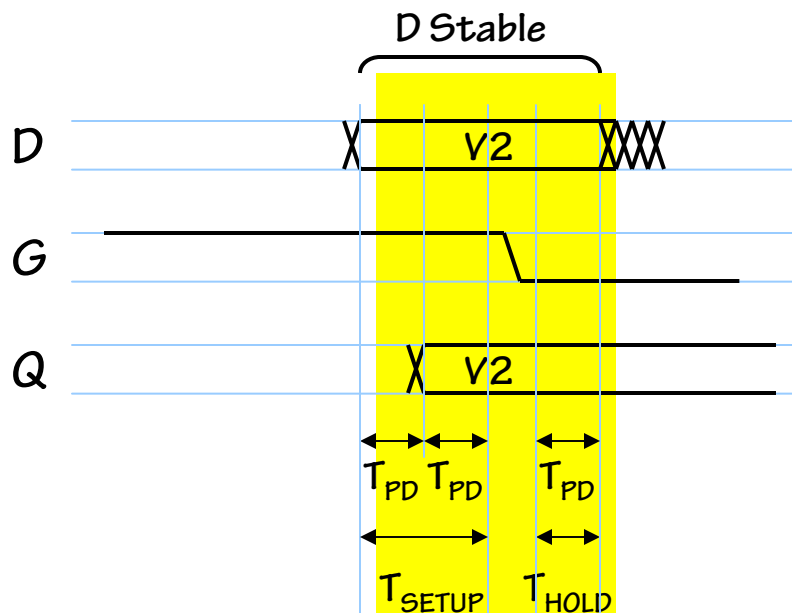 

To reliably latch V2:


- Apply V2 to D, holding $G=1$
- After T_{PD} , V2 appears at $Q=Q'$
- After another T_{PD} , Q' & D both valid for T_{PD} ; will hold $Q=V2$ independently of G
- Set $G=0$, while Q' & D hold $Q=D$
- After another T_{PD} , $G=0$ and Q' are sufficient to hold $Q=V2$ independently of D

Dynamic Discipline for our latch:

$T_{SETUP} = 2T_{PD}$: interval *prior to G* transition for which D must be stable & valid

$T_{HOLD} = T_{PD}$: interval *following G* transition for which D must be stable & valid

Lets try it out!

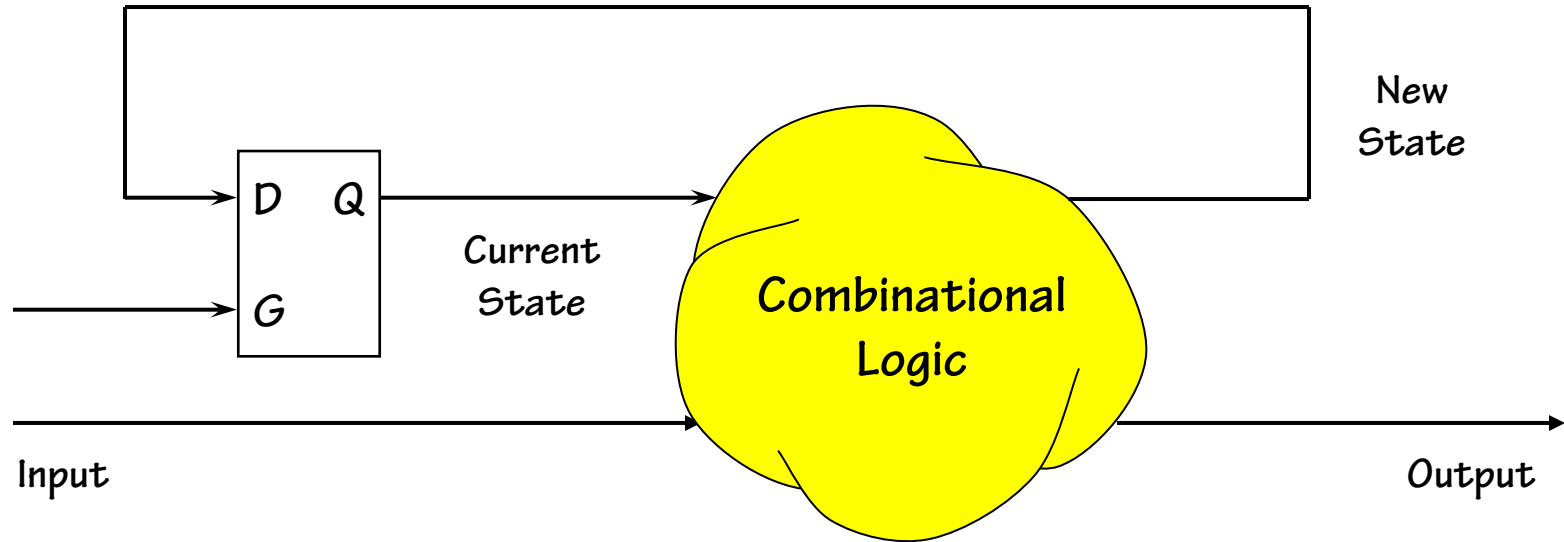


Plan: Build a Sequential Circuit with one bit of STATE –

- Single latch holds CURRENT state
- Combinational Logic computes
 - NEXT state (from input, current state)
 - OUTPUT bit (from input, current state)
- State changes when $G = 1$ (briefly!)

What happens
when $G=1$?

Combinational Cycles

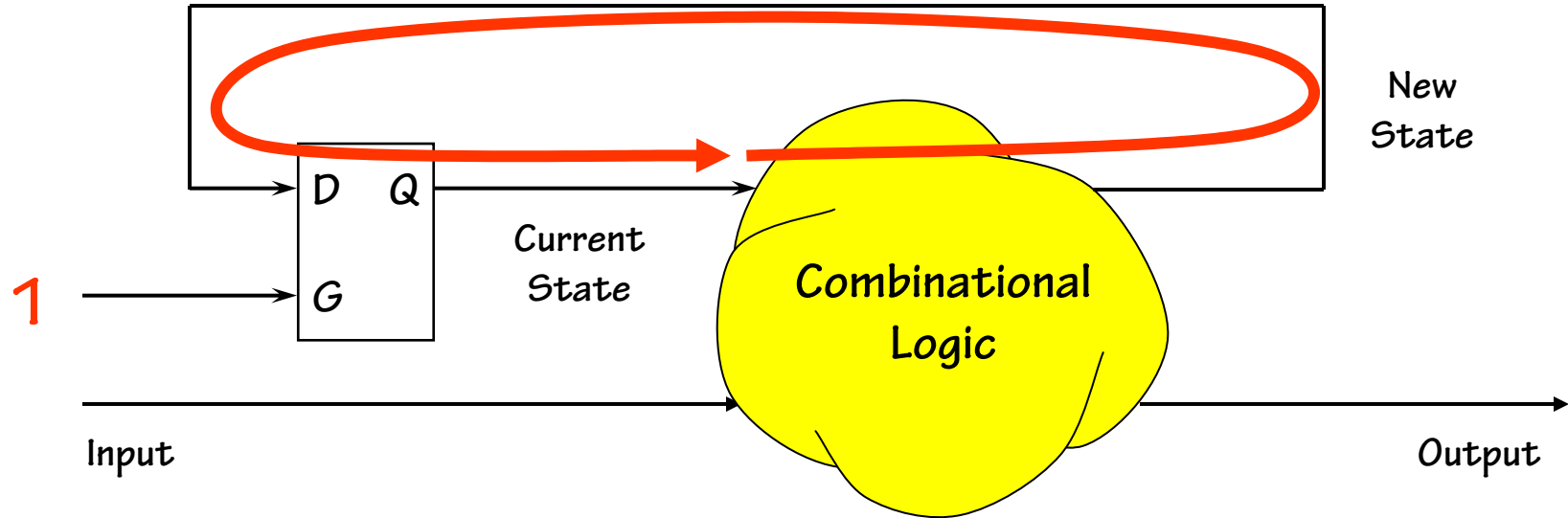

When $G=1$, latch is *Transparent*...

... provides a combinational path from D to Q.

Can't work without tricky timing constraints on $G=1$ pulse:

- Must fit within contamination delay of logic
- Must accommodate latch setup, hold times

Want to signal an *INSTANT*, not an *INTERVAL*...

Flakey Control Systems

Here's a strategy
for saving 2 bucks
on the Sumner
Tunnel!



Flakey Control Systems

Here's a strategy
for saving 2 bucks
on the Sumner
Tunnel



Flakey Control Systems

Here's a strategy
for saving 2 bucks
on the Sumner
Tunnel



Escapement Strategy

The Solution:
Add two gates
and only open
one at a time.



Escapement Strategy

The Solution:
Add two gates
and only open
one at a time.



Escapement Strategy

The Solution:
Add two gates
and only open
one at a time.



Escapement Strategy

The Solution:
Add two gates
and only open
one at a time.
(Psst... Don't
tell Massport)



Escapement Strategy

The Solution:
Add two gates
and only open
one at a time.
(Psst... Don't
tell Massport)



Escapement Strategy

The Solution:
Add two gates
and only open
one at a time.
(Psst... Don't
tell Massport)



Escapement Strategy

The Solution:
Add two gates
and only open
one at a time.
(Psst... Don't
tell Massport)



Escapement Strategy

The Solution:
Add two gates
and only open
one at a time.



Escapement Strategy

The Solution:
Add two gates
and only open
one at a time.



Escapement Strategy

The Solution:
Add two gates
and only open
one at a time.
(Psst... Don't
tell Massport)



Escapement Strategy

The Solution:
Add two gates
and only open
one at a time.
(Psst... Don't
tell Massport)




Escapement Strategy

The Solution:
Add two gates
and only open
one at a time.
(Psst... Don't
tell Massport)



Escapement Strategy

 The Solution:
Add two gates
and only open
one at a time.
(Psst... Don't
tell Massport)




Escapement Strategy

The Solution:
Add two gates
and only open
one at a time.




Escapement Strategy

 The Solution:
Add two gates
and only open
one at a time.




Escapement Strategy

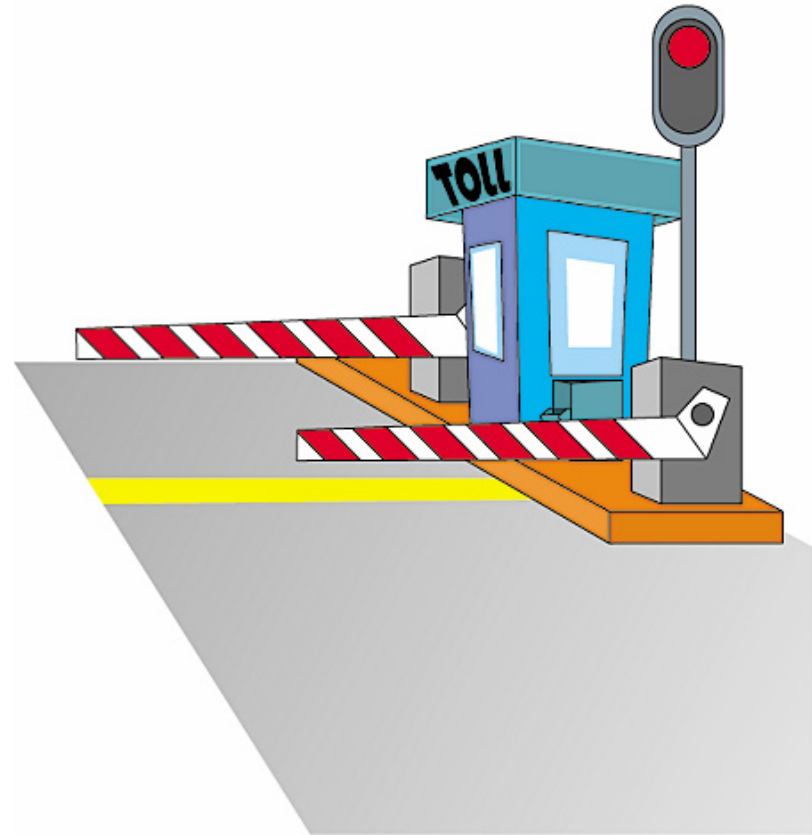The Solution:
Add two gates
and only open
one at a time.
(Psst... Don't
tell Massport)



KEY: At no time is there an open path
through both gates...

Edge-triggered Flip Flop

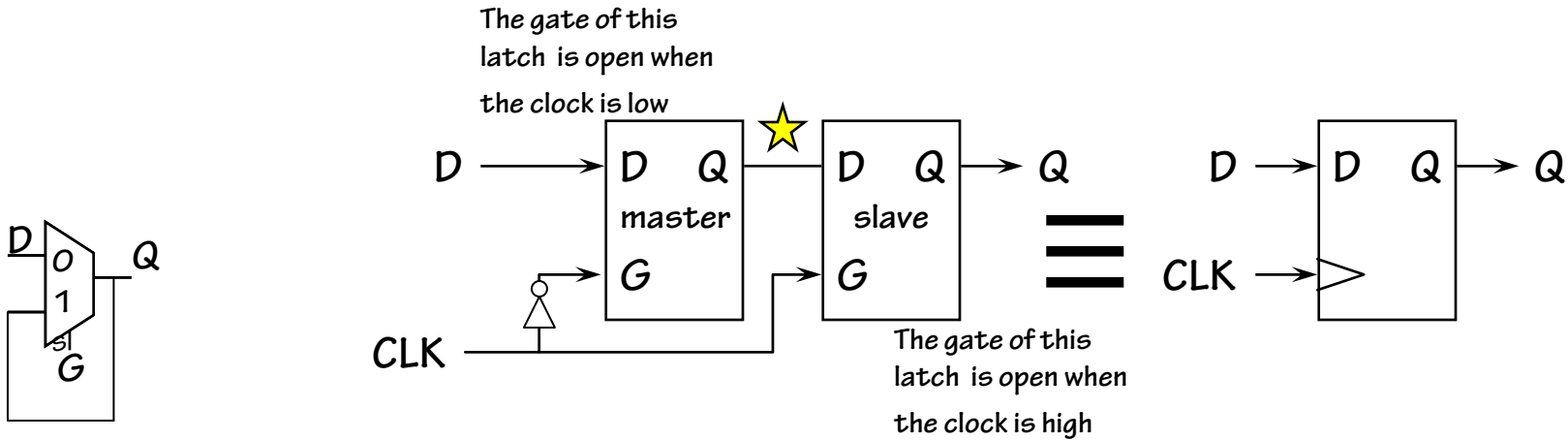

Observations:

- ♦ only one latch “transparent” at any time:

- ♦ master closed when slave is open


- ♦ slave closed when master is open

→ no combinational path through flip flop



(the feedback path in one of the master or slave latches is always active)

- ♦ Q only changes shortly after 0 → 1

 
transition of CLK, so flip flop **appears** to be “triggered” by rising edge of CLK



Flip Flop Waveforms

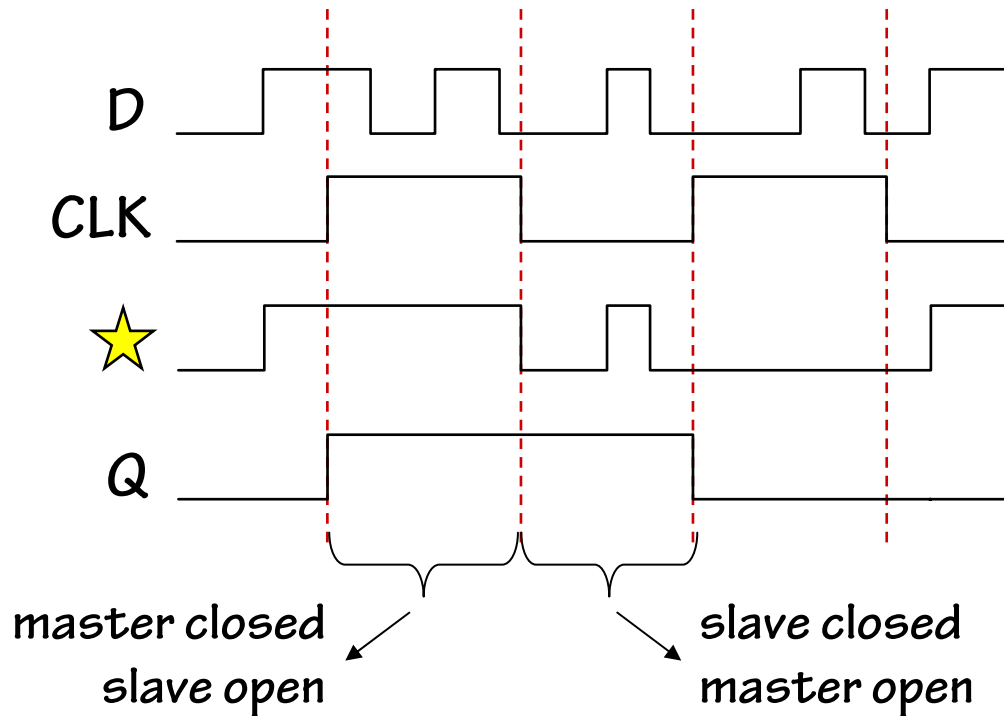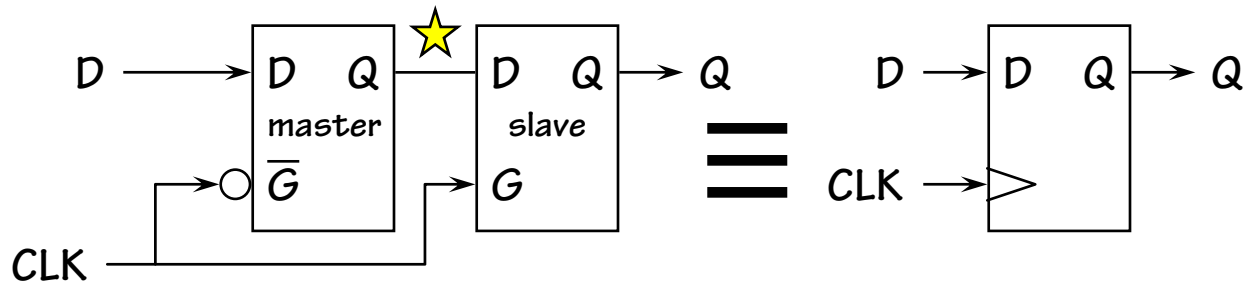

Um, about that hold time...


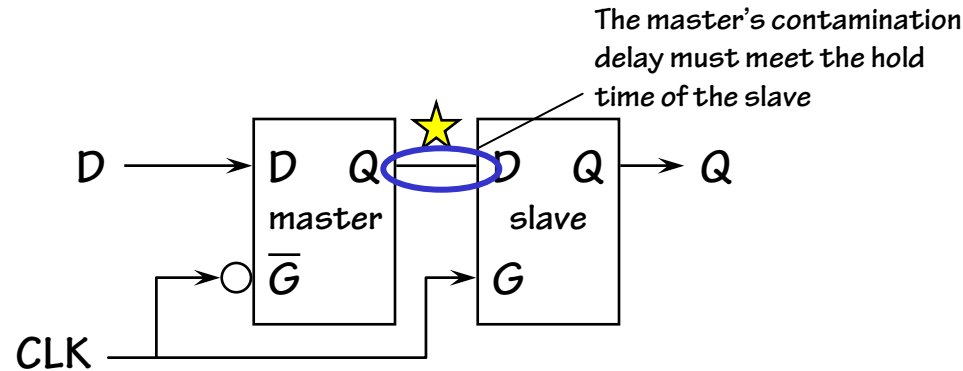


Consider HOLD TIME requirement for slave:

- Negative ($1 \rightarrow 0$) clock transition \rightarrow slave freezes data:
 - SHOULD be no output glitch, since master held constant data; BUT
 - master output contaminated by change in G input!
- HOLD TIME of slave not met, UNLESS we assume sufficient contamination delay in the path to its D input!

Accumulated t_{CD} thru inverter, $G \rightarrow Q$ path of master must cover slave t_{HOLD} for this design to work!

Flip Flop Timing - I

  

t_{PD} : maximum propagation delay, $CLK \rightarrow Q$

t_{CD} : minimum contamination delay, $CLK \rightarrow Q$

t_{SETUP} : setup time

guarantee that D has propagated through feedback path before master closes

t_{HOLD} : hold time

guarantee master is closed and data is stable before allowing D to change


Single-clock Synchronous Circuits



Does that
symbol
register?


We'll use Flip Flops and *Registers* – groups of FFs sharing a clock input – in a highly constrained way to build digital systems:

Single-clock Synchronous Discipline

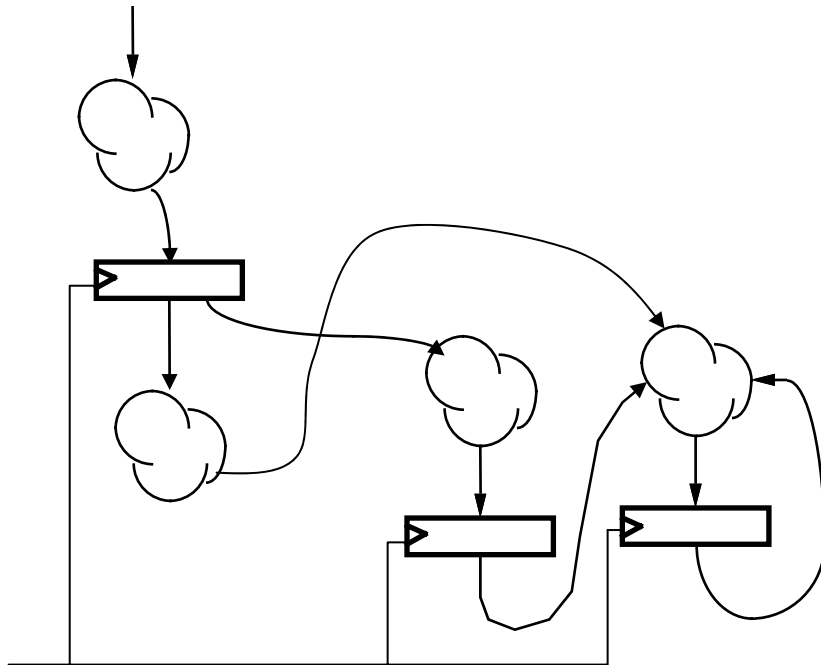

- No combinational cycles
- Single clock signal shared among all clocked devices
- Only care about value of combinational circuits just before rising edge of clock
- Period greater than every combinational delay
- Change saved state after noise-inducing logic transitions have stopped!

Flip Flop Timing - II

 


Questions for register-based designs:

- ◆ how much time for useful work (i.e. for combinational logic delay)?

- ◆ does it help to guarantee a minimum t_{CD} ? How 'bout designing registers so that

$$t_{CD,reg} > t_{HOLD,reg}?$$

 
- ◆ what happens if CLK signal doesn't arrive at the two registers at exactly the same time (a phenomenon known as "clock skew")?



$$t_1 = t_{CD,reg1} + t_{CD,1} > t_{HOLD,reg2}$$

$$t_2 = t_{PD,reg1} + t_{PD,1} < t_{CLK} - t_{SETUP,reg2}$$


Model: Discrete Time

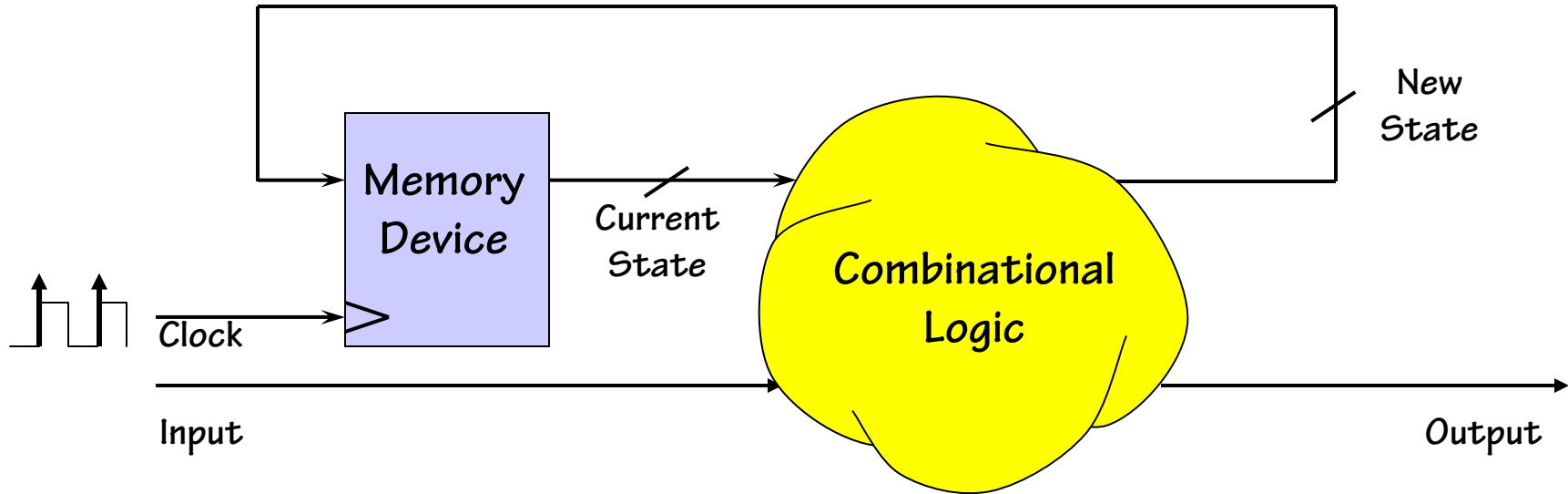

Active Clock Edges punctuate time ---

- Discrete Clock periods
- Discrete State Variables
- Discrete specifications (simple rules – eg tables – relating outputs to inputs, state variables)
- **ABSTRACTION: Finite State Machines (next lecture!)**

Sequential Circuit Timing

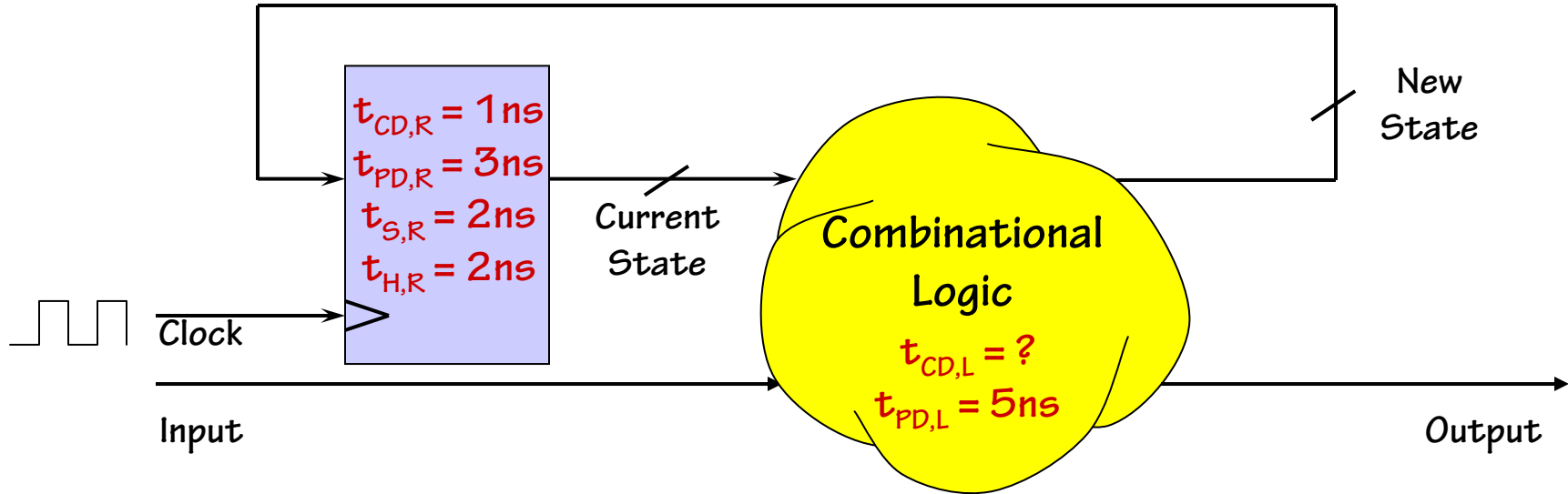

Questions:

- Constraints on T_{CD} for the logic? $> 1\text{ ns}$
- Minimum clock period? $> 10\text{ ns } (T_{PD,R} + T_{PD,L} + T_{S,R})$
- Setup, Hold times for Inputs?
 - $T_S = T_{PD,L} + T_{S,R}$
 - $T_H = T_{H,R} - T_{CD,L}$


This is a simple *Finite State Machine* ... more on Thursday!

Summary

"Sequential" Circuits (with memory):


Basic memory elements:

- Feedback, detailed analysis => basic level-sensitive devices (eg, latch)
- 2 Latches => Flop
- Dynamic Discipline: constraints on input timing

 

Synchronous 1-clock logic:

 - Simple rules for sequential circuits
- Yields clocked circuit with T_S, T_H constraints on input timing



Finite State Machines

Thursday's Topic!

